

**EE4530 Q1 of Semester 1, AY2014-15**

Typos in parts (b) and (c): Replace “Bus 1 and Bus 2” by “Bus 2 and Bus 3”.

(a)

$$\vec{Y}_{bus} = \begin{bmatrix} 17.94 - j26.92 & -7.69 + j11.54 & -10.25 + j15.38 \\ -7.69 + j11.54 & 23.10 - j34.65 & -15.41 + j23.11 \\ -10.25 + j15.38 & -15.41 + j23.11 & 25.66 - j38.49 \end{bmatrix} \text{ pu}$$

$$= \begin{bmatrix} 32.35 \angle -56.31^\circ & 13.87 \angle 123.69^\circ & 18.48 \angle 123.69^\circ \\ 13.87 \angle 123.69^\circ & 41.64 \angle -56.31^\circ & 27.78 \angle 123.69^\circ \\ 18.48 \angle 123.69^\circ & 27.78 \angle 123.69^\circ & 46.26 \angle -56.31^\circ \end{bmatrix} \text{ pu}$$

(b)

$$\vec{V}_2^1 = 0.935 \angle 0^\circ \text{ pu}, \vec{V}_3^1 = 0.915 \angle -0.684^\circ \text{ pu}$$

(c)

$$\vec{S}_1 = 5.991 \angle 51.496^\circ \text{ pu}, \vec{S}_G = 7.537 \angle 51.131^\circ \text{ pu}, \vec{S}_{L12} = 0.543 \angle 56.295^\circ \text{ pu}$$

**EE4530 Q1 of Semester 1, AY2013-14**

(a)

$$\vec{V}_2^1 = 0.99 \angle -0.772^\circ \text{ pu}, \vec{V}_3^1 = 1 \angle 0.0865^\circ \text{ pu}$$

Hint: Substitute the initial voltages in the GS equation to get  $\vec{V}_2^1$ . Using the new  $\vec{V}_2^1$ , compute  $Q_3^1$ . Next compute  $\vec{V}_3^1$ . You would notice that  $Q_3^1$  is within the given Q limits. This means that the magnitude of  $\vec{V}_3^1$  can be maintained/regulated at 1 pu.

(b)

$$\vec{S}_{12} = 0.266 + j0.2 \text{ pu}, \vec{S}_{13} = 0.00755 \text{ pu}$$

(c)

$$P_{G1} = \text{Real}(\vec{S}_{12} + \vec{S}_{13}) = 0.2742 \text{ pu}$$

At the end of iteration 1, the total active power generation =  $P_{G1} + P_{G3} = 0.2742 + 0.6 = 0.8742 \text{ pu}$ . However the total load active power =  $\text{Real}(0.8 + j0.6) = 0.8 \text{ pu}$ .

Since all the lines have no resistances, the line active power losses will be zero. For a lossless system, when the total active power generation of 0.8742 pu is not equal to the total load active power of 0.8 pu, the power flow solution has not converged. A difference between the supply and demand of 0.0742 pu (about 9.28% of load active power) is too big for a converged solution.

**EE4530 Q1 of Semester 1, AY2012-13**

(a)

$$\vec{S}_3 = (200 + j146.05) \text{ MVA}, Q_{G3} = 146.05 \text{ Mvar}$$

(b)

$$\vec{S}_{23} = (-228.93 - j148.01) \text{ MVA}, \vec{S}_{21} = (-171.07 - j102) \text{ MVA}$$

(c)

$$\vec{S}_{L23} = (9.842 + j19.685) \text{ MVA}$$