

### Example 1:

The one-line diagram of a three-phase power system is shown in Figure 1. Impedances are marked in per unit on a 100 MVA, 400 KV base. The load at bus 2 is  $S_2 = 15.93 \text{ MW} - j33.4 \text{ MVar}$ , and at bus 3 is  $S_3 = 77 \text{ MW} + j14 \text{ MVar}$ . It is required to maintain the voltage at bus 3 at 400kV. Determine the voltages at buses 2 and 1.

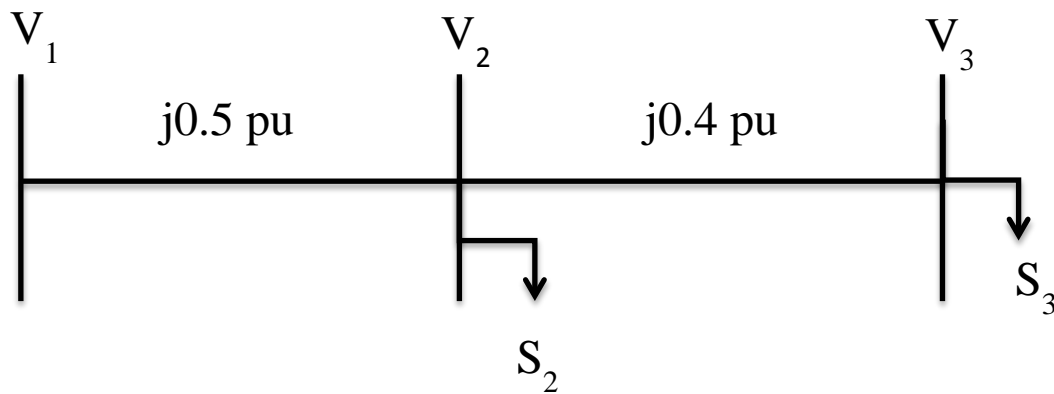


Figure 1 One-line diagram of Example 1

**Solution 1:** Using per unit to solve the problem

$$S_{\text{base}} = 100 \text{ MVA}, V_{\text{base}} = 400 \text{ kV}, V_3 = 1 \angle 0^\circ \text{ pu}$$

$$S_3 = 77 + j14 \text{ MVA} = 78.26 \angle 10.3^\circ \text{ MVA} = 0.7826 \angle 10.3^\circ \text{ pu}$$

$$S_2 = 15.93 - j33.4 \text{ MVA} = 37 \angle -64.5^\circ \text{ MVA}$$

$$= 0.37 \angle -64.5^\circ \text{ pu}$$

$$X_{23} = 0.4 \text{ pu and } X_{12} = 0.5 \text{ pu}$$

$$Q_3 = 0.14 \text{ pu}$$

The voltage at bus 2

$$V_2 = V_3 + \frac{X_{23}Q_3}{V_3} = 1 + \frac{0.4 \times 0.14}{1} = 1.056 \text{ pu}$$

The line voltage at bus 2

$$V_2 = 422.4 \text{ kV}$$

The magnitude of the current at bus 3 is

$$I_3 = S_3/V_3 = 0.7826 \text{ pu}$$

The reactive power loss during the power transmission from bus 2 to bus 3 is

$$Q_{\text{loss}} = I_3^2 \times X_{23} = 0.7826^2 \times 0.4 = 0.245 \text{ pu}$$

The total reactive power at bus 2

$$\begin{aligned} Q_2 &= \text{local load} + \text{power transferred} + \text{reactive power loss} \\ &= -0.334 + 0.14 + 0.245 = 0.051 \text{ pu} \end{aligned}$$

The voltage at bus 1

$$\begin{aligned} V_1 &= V_2 + \frac{X_{12}Q_2}{V_2} \\ &= 1.056 + \frac{0.5 \times 0.051}{1.056} = 1.08 \quad pu \end{aligned}$$

The line voltage at bus 1

$$V_1 = 432 \text{ kV}$$

**Solution 2:** Using the actual values (phase values) to do calculation.

$$S_3 = 78.26 \text{ MVA}$$

The phase reactive power and phase voltage at bus 3  
 $Q_3 = 4.667 \text{ MVar}$  and  $V_3 = 230.95 \text{ kV}$

Since  $Z_{\text{base}} = 1600 \Omega$ ,  $X_{23} = 640 \Omega$  and  $X_{12} = 800 \Omega$

The voltage at bus 2

$$\begin{aligned} V_2 &= V_3 + \frac{X_{23} Q_3}{V_3} = 230.95 + \frac{640 \times 4.667}{230.95} \\ &= 243.88 \text{ kV} \quad (\text{phase}) \end{aligned}$$

The line voltage at bus 2

$$V_2 = 422.4 \text{ kV}$$

The magnitude of the current at bus 3 is

$$I_3 = S_3 / (3V_3) = 78.26 / (3 \times 230.95) = 112.95 \text{ A}$$

The reactive power loss during the power transmission from bus 2 to bus 3 is

$$Q_{\text{loss}} = 3 I_3^2 \times X_{23} = 3 \times 112.95^2 \times 640 = 24.49 \text{ MVar}$$

The per phase reactive power at bus 2

$$\begin{aligned} Q_2 &= \text{local load} + \text{power transferred} + \text{reactive power loss} \\ &= (-33.4 + 14 + 24.49) / 3 = 1.7 \text{ MVar} \end{aligned}$$

The voltage at bus 1

$$\begin{aligned} V_1 &= V_2 + \frac{X_{12}Q_2}{V_2} \\ &= 243.88 + \frac{800 \times 1.7}{243.88} = 249.45 \quad kV \quad (\textit{phase}) \end{aligned}$$

The line voltage at bus 1

$$V_1 = 432 \text{ kV}$$

### Example 2:

The one-line diagram of a three-phase power system is shown in Figure 2. The transfer reactance is 20 percent on a base of 100 MVA, 23/115 kV and the line impedance is  $Z = j66.125 \Omega$ . The load at bus 2 is  $S_2 = 184.8 \text{ MW} + j6.6 \text{ MVar}$ , and at bus 3 is  $S_3 = + j20 \text{ MVar}$ . It is required to maintain the voltage at bus 3 at 115 kV. Determine the voltages at buses 2 and 1.

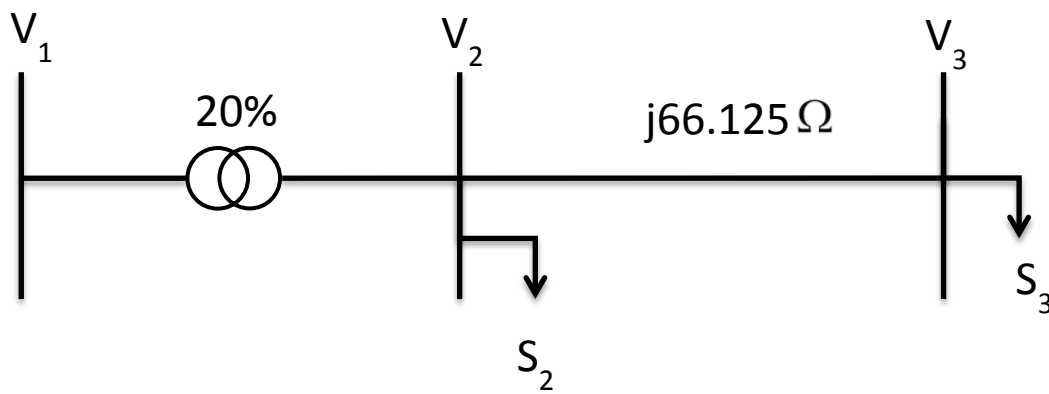


Figure 2 One-line diagram of Example 2

**Solution 1:** Using per unit to do calculation

$$S_{\text{base}} = 100 \text{ MVA}, V_{\text{base}} = 115 \text{ kV}, V_3 = 1 \angle 0^\circ \text{ pu}$$

$$S_3 = j20 \text{ MVar} = 0.2 \angle 90^\circ \text{ pu}$$

$$S_2 = 184.8 + j6.6 \text{ MVA} = 184.92 \angle 87.95^\circ \text{ MVA} \\ = 1.8492 \angle 87.95^\circ \text{ pu}$$

$$Z_{\text{base}} = \frac{V_{\text{base}}^2}{S_{\text{base}}} = \frac{115^2}{100} = 132.25 \quad \Omega$$

It follows that

$$X = \frac{X}{Z_{\text{base}}} = \frac{66.125}{132.25} = 0.5 \quad pu$$

$$X = 0.5 \text{ pu and } X_T = 0.2 \text{ pu. } Q_3 = j20 \text{ MVar} = 0.2 \text{ pu}$$

The voltage at bus 2

$$V_2 = V_3 + \frac{X Q_3}{V_3} = 1 + \frac{0.5 \times 0.2}{1} = 1.1 \quad pu$$

$$V_2 = 126.5 \text{ kV.}$$

The magnitude of the current at bus 3 is

$$I_3 = S_3/V_3 = 0.2 \text{ pu}$$

The reactive power loss during the power transmission from bus 2 to bus 3 is

$$Q_{\text{loss}} = I_3^2 \times X_{23} = 0.2^2 \times 0.5 = 0.02 \text{ pu}$$

The total reactive power at bus 2

$$Q_2 = 0.066 + 0.2 + 0.02 = 0.286 \text{ pu}$$

The voltage at bus 1

$$V_1 = V_2 + \frac{X_T Q_2}{V_2} = 1.1 + \frac{0.2 \times 0.286}{1.1} = 1.152 \text{ pu}$$

$$V_1 = 26.5 \text{ kV.}$$



**Solution 2:** Using the actual values (phase values) to do calculation.

$$S_3 = j20 \text{ MVar}$$

The phase reactive power and phase voltage at bus 3  
 $Q_3 = 6.667 \text{ MVar}$  and  $V_3 = 66.4 \text{ kV}$

Since  $Z_{\text{base}} = 132.25 \Omega$ ,  $X_{23} = 66.125 \Omega$  and  $X_{12} = 26.45 \Omega$  at 115 kV side (or  $X_{12} = 1.058 \Omega$  at 23 kV side ( $Z_{\text{base}} = 5.29 \Omega$ ))

The voltage at bus 2

$$\begin{aligned} V_2 &= V_3 + \frac{X_{23} Q_3}{V_3} = 66.4 + \frac{66.125 \times 6.667}{66.4} \\ &= 73.04 \text{ kV} \end{aligned}$$

The line voltage at bus 2

$$V_2 = 126.5 \text{ kV}$$

The magnitude of the current at bus 3 is

$$I_3 = S_3 / (3V_3) = 20 / (3 \times 66.4) = 100.4 \text{ A}$$

The reactive power loss during the power transmission from bus 2 to bus 3 is

$$Q_{\text{loss}} = 3 I_3^2 \times X_{23} = 3 \times 100.4^2 \times 66.125 = 2 \text{ MVar}$$

The per phase reactive power at bus 2

$$\begin{aligned} Q_2 &= \text{local load} + \text{power transferred} + \text{reactive power loss} \\ &= (6.6 + 20 + 2) / 3 = 9.533 \text{ MVar} \end{aligned}$$

The voltage at bus 1

$$\begin{aligned} V_1 &= V_2 + \frac{X_{12}Q_2}{V_2} \\ &= 73.04 + \frac{26.45 \times 9.533}{73.04} = 76.5 \text{ kV} \end{aligned}$$

The line voltage at bus 1

$$V_1 = \frac{\sqrt{3} \times 76.5 \times 23}{115} = 26.5 \text{ kV}$$

### Example 3:

A 11 kV line is fed through an 11kV/415V transformer from a constant 11 kV supply, as shown in Figure 3. The total impedance of the line and transformers at 11 kV is  $(1.2 + j 3.6) \Omega$ . The transformer is equipped with tap-changing facility (t:1). If the load on the system is 1.08 MW and 0.81 MV<sub>AR</sub>, determine the tap ratio of the transformer if the receiving-end voltage is to be maintained at 415 V. Use a base of 1 MVA, 11 kV.

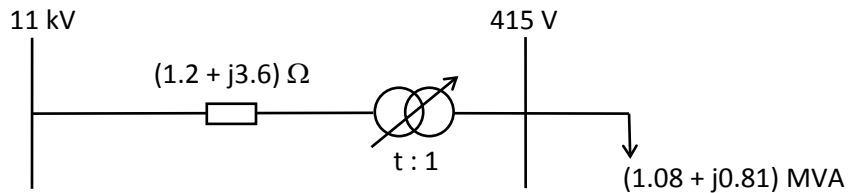


Figure 3 The system in Example 3

**Solution 1:** Using per unit to do calculation

The bases:  $S_{base} = 1 \text{ MVA}$ ,  $V_{base} = 11 \text{ kV}$

It gives that  $P = 1.08 \text{ pu}$ ,  $Q = 0.81 \text{ pu}$  and  $V_S = V_R = 1 \text{ pu}$

$$Z_{base} = \frac{V_{base}^2}{S_{base}} = \frac{11^2}{1} = 121 \quad \Omega$$

It follows that

$$R = \frac{R}{Z_{base}} = \frac{1.2}{121} = 0.00992 \quad pu$$

$$X = \frac{X}{Z_{base}} = \frac{3.6}{121} = 0.02975 \quad pu$$

$$\Delta V = \frac{V_S}{t} - V_R = \frac{RP + XQ}{t^2 V_R}$$

It gives that

$$t^2 V_R^2 - t V_S V_R + (RP + XQ) = 0$$

$$t^2 - t + (0.00992 \times 1.08 + 0.02975 \times 0.81) = 0$$

$$\therefore t = \frac{1 + 0.9278}{2} = 0.964$$

The tap ratio of the transformer  $t = 0.964$ .

**Solution 2:** Using phase values or line values to do calculation

$$R = 1.2 \, \Omega \text{ and } X = 3.6 \, \Omega$$

$$P = 1.08 \text{ MW (3-phase)} = 0.36 \text{ MW (1-phase)}$$

$$Q = 0.81 \text{ MV}_{AR} \text{ (3-phase)} = 0.27 \text{ MW (1-phase)}$$

$$V_S = 11 \text{ kV (line)} = 6.35 \text{ kV (phase)}$$

$$V_R = 415 \text{ V (line)} = 239.61 \text{ V (phase)}$$

The turn ratio,  $a$ , is 11kV/415V

It follows that

$$\Delta V = \frac{V_S}{ta} - V_R = \frac{RP + XQ}{t^2 a^2 V_R}$$

**Line values:**  $V_R$  and  $V_S$  should be line values and  $P$  and  $Q$  are three phase powers.

$$t^2 a^2 V_R^2 - ta V_S V_R + (RP + XQ) = 0$$

$$t^2 (11k / 415)^2 \times 415^2 - t(11k / 415) 11k \times 415 + (1.2 \times 1.08 + 3.6 \times 0.81) = 0$$

$$t^2 - t + \frac{(1.2 \times 1.08 + 3.6 \times 0.81)}{(11k)^2} = 0$$

$$\therefore t = \frac{1 + 0.9278}{2} = 0.964$$

**Phase values:**  $V_R$  and  $V_S$  should be phase values and  $P$  and  $Q$  are single phase powers.

$$t^2 a^2 V_R^2 - t a V_S V_R + (RP + XQ) = 0$$

$$\begin{aligned} t^2 \left( \frac{11k}{415} \right)^2 \times (239.607)^2 - t \left( \frac{11k}{415} \right) \times 6.35k \times 239.61 \\ + (1.2 \times 0.36 + 3.6 \times 0.27) = 0 \\ t^2 - t + \frac{(1.2 \times 0.36 + 3.6 \times 0.27)}{(11k)^2 / (\sqrt{3})^2} = 0 \end{aligned}$$

$$\therefore t = \frac{1 + 0.9278}{2} = 0.964$$

The tap ratio of the transformer  $t = 0.964$ .