

a) $\mathbf{Y}_{bus} = \begin{bmatrix} 5.882352941 - j23.42941176 & -5.882352941 + j23.52941176 \\ -5.882352941 + j23.52941176 & 5.882352941 - j23.42941176 \end{bmatrix}$ *

b) $S_z = -1 - j0.5$

$$V_z' = \left[\left(\frac{S_z}{V_z^0} \right)^* - V_1 Y_{z1} \right] \frac{1}{Y_{zz}} = 0.973859318 - j0.036118332$$
 *

c) $\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$

$$\begin{aligned} S_1 &= V_1 I_1^* = V_1 [Y_{11} V_1 + Y_{12} V_2]^* \\ &= 1.012294117 + j0.35467647 \end{aligned}$$

$$\begin{aligned} S_{loss} &= P_{loss} + jQ_{loss} = S_1 + S_z \\ &= 0.012294117 - j0.145323529 \end{math} *$$

$$\begin{aligned} S_{G1} &= S_1 + S_{D1} \\ &= 1.212294117 + j0.40467647 \end{aligned}$$
 *

d) $I_{12} = (V_1 - V_2)/Z_{12} = 1.012294118 - j0.45467647$

$$I_{10} = V_1 Y_{10} = j0.1$$

$$I_{20} = V_2 Y_{20} = 0.0035945 + j0.097169$$

$$Q_{10} = |I_{10}|^2 \times \frac{-1}{0.1} = -0.1$$

$$Q_{20} = |I_{20}|^2 \times \frac{-1}{0.1} = -0.094547349$$

$$Q_{12} = |I_{12}|^2 \times 0.04 = 0.049258802$$

$$Q_{loss} = -0.145288546$$

\approx same as Q_{loss} from (c)

$$Q_{loss} + Q_{D1} + Q_{D2} = 0.404711453 \approx \text{same as } Q_g \text{ from (c)}$$
 *

$$2a) \Delta P_{tieA} = \beta_A \Delta f - 0 = 10 \Rightarrow \beta_A \Delta f = 10$$


$$\Delta P_{tieB} = \beta_B \Delta f - 50 = -10 \Rightarrow \beta_B \Delta f = 40$$

$$\Rightarrow \Delta f = \frac{10}{\beta_A} \Rightarrow \beta_B = 4\beta_A \quad -①$$

After trip,

$$\Delta f_A = \frac{-(-10)}{\beta_A} = \frac{10}{\beta_A}$$
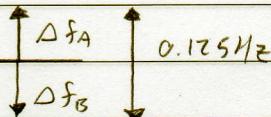
$$\Delta f_B = \frac{-(10)}{\beta_B} = \frac{-10}{\beta_B}$$



$$\Delta f_A - \Delta f_B = \frac{10}{\beta_A} + \frac{10}{\beta_B} = 0.125 \quad -②$$

Sub ① into ②,

$$\frac{10}{\beta_A} + \frac{10}{4\beta_A} = 0.125$$

$$\frac{12.5}{\beta_A} = 0.125 \Rightarrow \beta_A = 100 \text{ MW/Hz} \quad \#$$

$$\beta_B = 400 \text{ MW/Hz} \quad \#$$

b) $ICR_1 = 5 + 0.016P_1$
 $ICR_2 = 5.5 + 0.018P_2$
 $ICR_3 = 4.5 + 0.014P_3$
 $P_o = 550 \text{ MW}$

i) $P_1 = (\lambda - 5)/0.016$
 $P_2 = (\lambda - 5.5)/0.018$
 $P_3 = (\lambda - 4.5)/0.014$

$$P_1 + P_2 + P_3 = P_o$$

$$(\lambda - 5)/0.016 + (\lambda - 5.5)/0.018 + (\lambda - 4.5)/0.014 = 550$$

$$62.5\lambda - 312.5 + 55.6\lambda - 305.6 + 71.4\lambda - 321.4 = 550$$

$$\Rightarrow 189.5\lambda = 1489.5$$

$$\lambda = 7.86$$

$$\Rightarrow P_1 = 178.8 \text{ MW} \cancel{\text{#}}$$

$$\Rightarrow P_2 = 131.1 \text{ MW} \cancel{\text{#}}$$

$$\Rightarrow P_3 = 240.0 \text{ MW} \cancel{\text{#}}$$

ii) Since $P_2 < P_{2\min}$, \therefore Set $P_2 = 150 \text{ MW}$
 $P_1 + 150 + P_3 = 550 \Rightarrow P_3 = 400 - P_1 \text{ -①}$

$$ICR_1 = ICR_3$$

$$5 + 0.016P_1 = 4.5 + 0.014P_3 \text{ -②}$$


Sub ① into ②,

$$5 + 0.016P_1 = 4.5 + 0.014(400 - P_1)$$

$$\Rightarrow P_1 = 170 \text{ MW} \cancel{\text{#}}$$

$$P_3 = 230 \text{ MW} \cancel{\text{#}}$$
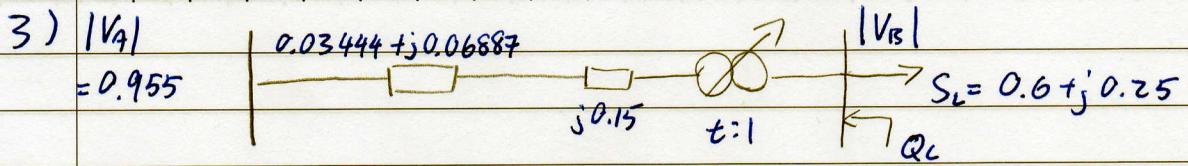
$$\& P_2 = 150 \text{ MW} \cancel{\text{#}}$$



$S_b = 20 \text{ MVA}$

$V_{b1} = 66 \text{ kV}$

$Z_{b1} = 217.8 \Omega$

$, V_{b2} = 11 \text{ kV}$

a) $|V_B| = 1, Q_C = 0,$

$|V_A| - t|V_B| = \frac{RP + QX}{t|V_B|}$

$0.955 - t = \frac{(0.03444)(0.6) + (0.25)(0.15 + 0.06887)}{t}$

$t^2 + -0.955t + 0.0753815 = 0$

$\Rightarrow t = 0.868, 0.0868 \text{ (reject)}$

b) When $t = 1, Q_C = 0,$

Since $|V_A|, R, P, Q, X$ is fix, $t|V_B|$ must also be constant.

$\text{Let } k = t|V_B|,$

$k^2 - 0.955k + 0.0753815 = 0$

$\Rightarrow k = 0.868, 0.0868 \text{ (reject)}$

$\Rightarrow t|V_B| = 0.868$

$S_{\text{loss}} = |I_A|^2 \times Z_{\text{loss}}, |I_A|^2 = \frac{P_L^2 + Q_L^2}{t^2 |V_B|^2}$

$\therefore |I_A|^2 = 0.561$

$\Rightarrow P_{\text{loss actual}} = |I_A|^2 \times (0.03444) \times S_b = 0.386 \text{ MW} \times$

$Q_{\text{loss actual}} = |I_A|^2 \times (0.15 + 0.06887) \times S_b = 2.455 \text{ M Var} \times$

Since $t|V_B| = 0.868, \therefore |I_A|^2$ is always constant. Hence the loss cannot be reduced if the tap changing transformer is installed. \times

$$c) t = 0.9, |V_B| = 1$$

$$|V_A| - t|V_B| = \frac{RP + X(Q_L - Q_C)}{t|V_B|}$$

$$0.955 - 0.9 = \frac{(0.03444)(0.6) + (0.15 + 0.06887)(0.25 - Q_C)}{0.9}$$

$$Q_C = 0.11825$$

$$\Rightarrow Q_{C\text{ actual}} = Q_C \times S_b = 2.365 \text{ MVar} \cancel{\text{xx}}$$

$$4a) Z_1 = j0.2 + j0.21 + j(0.84)/2 = j0.83$$

$$I_o = (S_o/V_o)^* = 1.02 \angle -11.3^\circ$$

$$E = V_o + I_o Z_1 = 1.43 \angle 35.4^\circ$$

$$\therefore P_{e1} = \left| \frac{E' V_o}{Z_1} \right| \sin \delta = 1.724 \sin \delta \text{ A}$$


$$b) \delta_c = 900 \times (0.1)^2 + 35.4^\circ \\ = 44.4^\circ$$

$$Z_2 = P_{e2} = 0$$

$$Z_3 = j0.2 + j0.21 + j0.84 = j1.25$$

$$P_{e3} = \left| \frac{E' V_o}{Z_3} \right| \sin \delta = 1.144 \sin \delta$$
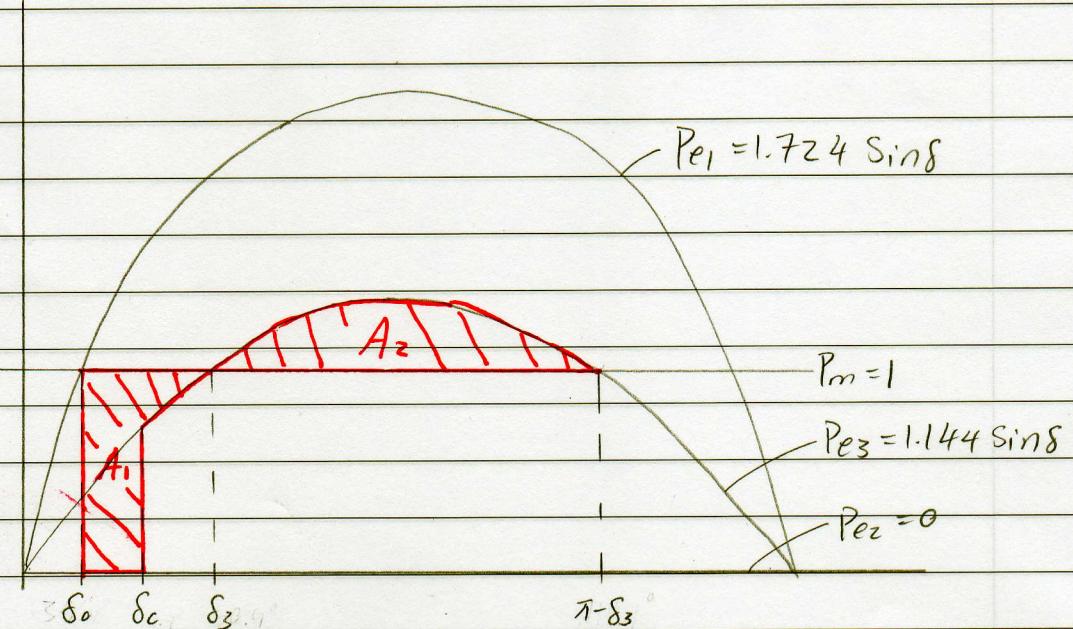
$$\delta_3 = \sin^{-1} \left(\frac{1}{1.144} \right) = 60.9^\circ$$



$$\delta_0 = 35.4^\circ$$

$$\delta_c = 44.4^\circ$$

$$\delta_3 = 60.9^\circ$$

$$\pi - \delta_3 = 119.1^\circ$$

$$A_1 = \int_{\delta_0}^{\delta_c} (P_m - P_{e2}) d\delta + \int_{\delta_c}^{\delta_3} (P_m - P_{e3}) d\delta$$

$$= \int_{\delta_0}^{\delta_c} (1) d\delta + \int_{\delta_c}^{\delta_3} (1 - 1.144 \sin \delta) d\delta$$

$$= [\delta]_{\delta_0}^{\delta_c} + [\delta + 1.144 \cos \delta]_{\delta_c}^{\delta_3}$$

$$= [0.157] + [0.02699]$$

$$= 0.184$$

$$A_2 = \int_{\delta_3}^{\pi - \delta_3} (P_{e3} - P_m) d\delta$$

$$= \int_{\delta_3}^{\pi - \delta_3} (1.144 \sin \delta - 1) d\delta$$

$$= [-1.144 \cos \delta - \delta]_{\delta_3}^{\pi - \delta_3}$$

$$= 0.097$$

$A_1 > A_2 \therefore \text{Unstable. } \textcolor{red}{X}$